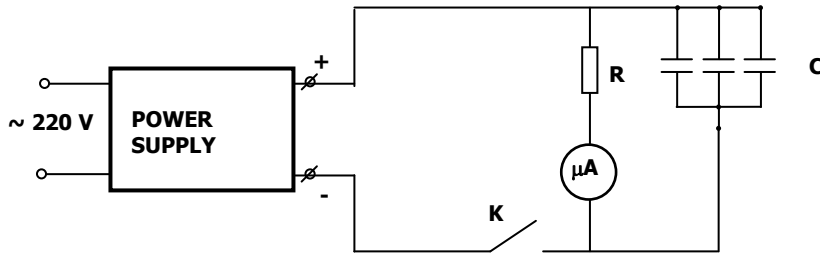


12 - RELAXATION PROCESSES IN ELECTRICAL CIRCUITS

I. Capacitor charging (discharging) process analysis




1. Build the circuit shown in the figure alongside. Close the switch K for a brief moment to charge the capacitor and open the switch starting the process of the capacitor discharging (C – electrolytic capacitor 100 μF , R – resistor 100 $\text{k}\Omega$).
2. Measurements of the charging current (or discharging) read every 5 seconds should be written in the table. R and C accuracy is 1%.

C [μF]	R [$\text{k}\Omega$]	I ₀ [μA]	T [s]					
			0	5	10	15	20	25...
C ₁ =	R ₁ =							
	R ₂ =							
C ₂ =	R ₁ =							
	R ₂ =							

3. Stop the measurements after the time $t=3\tau$ when the current value falls to about 5% of the initial value.

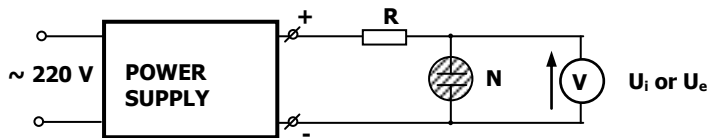
II. Measurement of ignition U_i and extinction U_e voltages of neon lamp



1. Build the circuit shown in the figure alongside (R=50 $\text{k}\Omega$). Use the **digital voltmeter (range 100 V, DC)** to measure voltage.
2. Turn the voltage knob on the power supply very slowly to increase the voltage till the moment the lamp ignites.
3. Write down the highest voltage read **BEFORE** the ignition, U_i (when the lamp ignites, the voltage falls by a dozen or so volts to the so-called maintaining voltage).


4. Reduce the voltage and write down U_e voltage at each the gas stops glowing. Repeat the measurement several times, and write down the results in table. Calculate their average values. Consider the uncertainties type A and B.

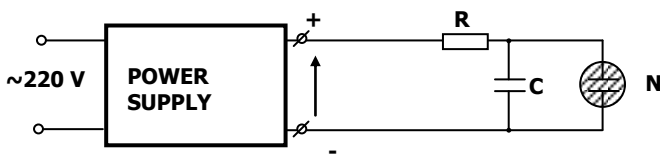III. Analysis of oscillation period dependence with respect to resistance R and capacitance C



1. Build the circuit shown in the figure alongside (C – capacitors 2 μF , 1 μF i 0.47 μF , R – resistors from 300 to 850 $\text{k}\Omega$).
2. Set such a voltage U, to see neon lamp flashing for each measured resistance R (the power supply voltage has to remain constant during the measurement).
3. Measure at least twice time of $n=20$ flashes of neon lamp for various subsequent R values. The measurement result and the calculated oscillation period have to be written in table. R and C accuracy is 5%.

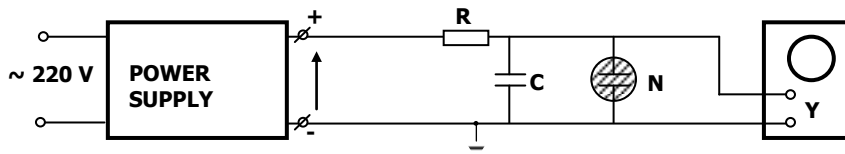IV. Observation of relaxation oscillation on the oscilloscope screen



1. Build a circuit shown above. Make sure to connect correctly the GND terminal of the power supply and the oscilloscope, and to use in the circuit a resistor R of a lower resistance.
2. Basing on observations of the waveform in the screen, estimate the capacitor's charging and discharging times.

NOTICE: DIGITAL VOLTMETERS ACCURACY:

V530, V531, V541, V543, V544: $c_1 = 0,05\%$; $c_2 = 0,01\%$ (for all DC voltage ranges)